 


VLSI Design
Homework 1 SOLUTIONS

Description: This assignment will survey what you have learned thus far using problems from R. Baker's "CMOS Circuit Design, Layout, and Simulation"

Associated Reading Material:

Chapters 5 (Sections 5.1-5.3), 6 (Entire Chapter), 7 (Entire Chapter), 11 (Sections 11.1-11.3), and 12 (Sections 12.1-12.3)



5.7 (Layout-to-Schematic Analysis)

TBA

6.4 (MOS capacitance): If the oxide thickness of a MOSFET is 40 Å. What is C'_{ox} ?

Solution:

$$C'_{ox} = \epsilon_{ox}/T_{ox} = (8.85 \times 3.97 \text{ aF}/\mu\text{m})/(40 \times 10^{-10} \text{ m}) = \mathbf{8.784 \text{ fF}/\mu\text{m}^2}$$

6.12 (Channel resistance): Using Eq. (6.35) estimate the small-signal channel resistance (the change in the drain current with changes in the drain-source voltage) of a MOSFET operating in the triode region (the resistance between the drain and source).

Solution:

$$\text{Eq 6.35: } I_D = \beta^* [(V_{gs} - V_{thn})V_{ds} - V_{ds}^2/2]$$

$$r = \Delta V_{ds} / \Delta I_D$$


$$= (V_{ds1} - V_{ds2}) / [(\beta^* [(V_{gs} - V_{thn})(V_{ds1}) - (V_{ds1})^2/2] - \beta^* [(V_{gs} - V_{thn})(V_{ds2}) - (V_{ds2})^2/2])]$$

$$= (V_{ds1} - V_{ds2}) / [(\beta^* [(V_{gs} - V_{thn})(V_{ds1} - V_{ds2}) - (V_{ds1})^2/2 + (V_{ds2})^2/2])]$$

$$= 1 / [(\beta^* [(V_{gs} - V_{thn}) - (V_{ds1} + V_{ds2})/2])]$$

$$\mathbf{r = 1 / [\beta^*(V_{gs} - V_{thn} - V_{ds})]}$$

 6.13 (Parallel MOSFET Connections): Show, using Eqs. 6.33 and 6.37, that the parallel connection of MOSFETs shown in Fig. 5.18 behaves as a single MOSFET with a width equal to the sum of the individual MOSFET's widths.



Equivalent of Fig. 5.18

Solution: From Kirchoff's Current Law, we know that $I_d = I_{d1} + I_{d2} + I_{d3} + I_{d4}$. So if each MOSFET has the same KP , L , V_{GS} , V_{DS} and V_{THN} , equations 6.33 and 6.37 become:


$$I_d = KP_n \cdot \frac{W1 + W2 + W3 + W4}{L} \cdot \left[(V_{GS} - V_{THN})V_{DS} - \frac{V_{DS}^2}{2} \right] \quad \text{for Eq. 6.33}$$

$$I_d = KP_n \cdot \frac{W1 + W2 + W3 + W4}{L} \cdot \left[(V_{GS} - V_{THN})^2 \right] \quad \text{for Eq. 6.37}$$

This shows that the total drain current, I_d , is equal to a single MOSFET with a width equal to $W1 + W2 + W3 + W4$.

6.15 (Series MOSFET Connections): Show that the series connection of MOSFETs shown in fig. 6.21 behaves as a single MOSFET with Twice the length of the individual MOSFETs. Again neglect the body effect.

Solution:

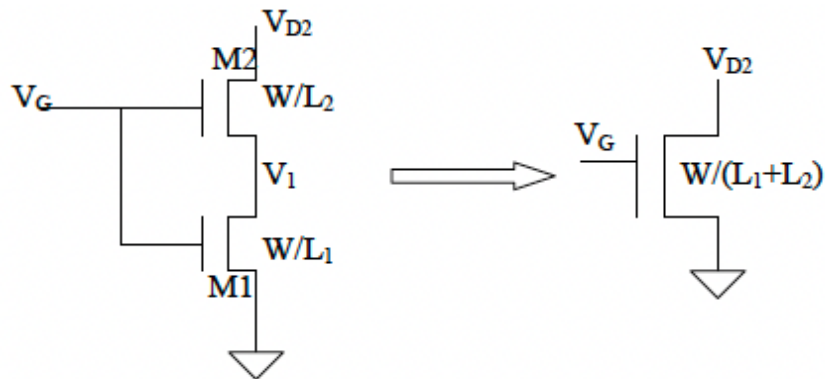

Assuming both MOSFETs are in triode region

For M₁ $I_{D1} = I_D$

$$I_{D1} = I_D = K P_n (W/L_1) [(V_G - V_{THN})V_1 - V_1^2/2]$$

$$(I_D L_1) / (K P_n W) = [(V_G - V_{THN})V_1 - V_1^2/2]$$

As Both MOSFETs are in series i.e., $I_{D1} = I_{D2} = I_D$

For M₂ $I_{D2} = I_D$

$$I_{D2} = I_D = K P_n (W/L_2) [(V_G - V_1 - V_{THN})(V_{D2} - V_1) - (V_{D2} - V_1)^2/2]$$

$$(I_D L_2) / (K P_n W) = [(V_G - V_1 - V_{THN})(V_{D2} - V_1) - (V_{D2} - V_1)^2/2]$$

$$[(I_D L_1) / (K P_n W)] + [(I_D L_2) / (K P_n W)] = [(V_G - V_{THN})V_1 - V_1^2/2] + [(V_G - V_1 - V_{THN})(V_{D2} - V_1) - (V_{D2} - V_1)^2/2]$$

$$[(I_D (L_1 + L_2)) / (K P_n W)] = [(V_G - V_{THN}) V_{D2} - (V_{D2})^2/2]$$

This is the current from drain to source for a single MOSFET with length $(L_1 + L_2)$

If $L_1 = L_2 = L$

$$[(2I_D L) / (K P_n W)] = [(V_G - V_{THN}) V_{D2} - (V_{D2})^2/2]$$

$$I_D = [(K P_n W) / 2L] [(V_G - V_{THN}) V_{D2} - (V_{D2})^2/2]$$

7.4 (Ion Implantation)

TBA

7.10 (Metal Deposition)

TBA

11.1 (Inverter DC Characteristics)

Solution:

From the graphs in Fig. 11.4 and the text in p11.3, we have $V_{OH} =$

V_{OL}	$= 0V$	Process	Long channel
V_{IL}	$= 1.8V$		
V_{IH}	$= 2.1V$		

Therefore, noise margins,
 $NM_H = V_{OH} - V_{IH} = 5 - 2.1 = 2.9V$
 $NM_L = V_{IL} - V_{OL} = 1.8 - 0 = 1.8V$

For the short channel process, similarly from the graph and text in the book, $V_{OH} =$


1V
 $V_{OL} = 0V$
 $V_{IL} = 400mV$
 $V_{IH} = 500mV$

So, noise margins,
 $NM_H = V_{OH} - V_{IH} = 1 - 0.5 = 0.5V = 500mV$
 $NM_L = V_{IL} - V_{OL} = 0.4 - 0 = 0.4V = 400mV$

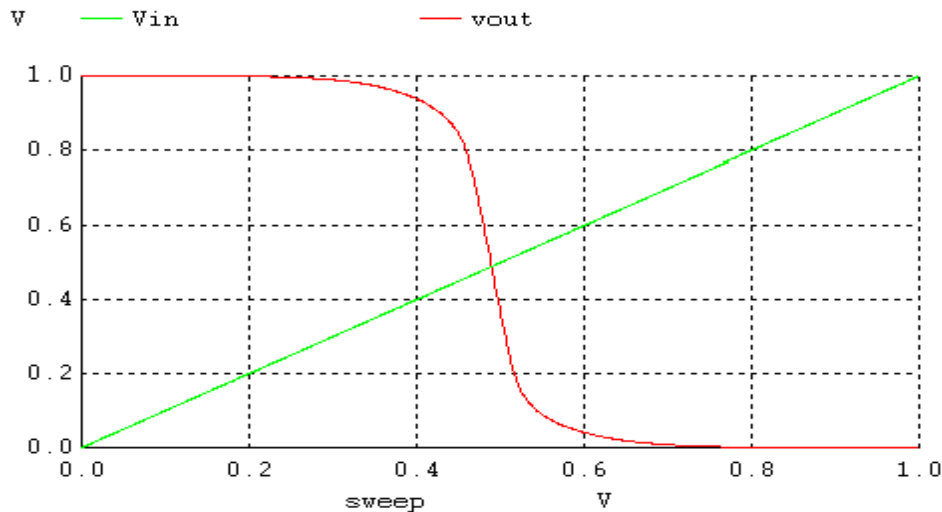11.3 (Inverter Switching Point): Show that the switching point of three inverters in series is dominated by the V_{sp} of the first inverter.


Solution: Three inverters with different switching points are simulated as below:

```
*Stage1 Inverter
.control
destroy all
run
let Icross=-i(vdd)
*plot Icross
plot vout Vin
.endc
.option scale=50n
.dc vin 0 1 1m
vdd      vdd      0      DC      1
Vin      vin      0      DC      0
M1       vout     vin     0      0      NMOS L=1 W=10
M2       vout     vin     vdd     vdd    PMOS L=1 W=20
* 50nm BSIM4 models
```




Stage2 and 3 Inverters with different Switching points:
 
```
*Stage2 Inverter
.control destroy all run
let Icross=-i(vdd)
*plot Icross plot vout Vin
.endc
.option scale=50n
.dc vin 0 1 1m
vdd      vdd      0      DC      1
Vin      vin      0      DC      0
M1       vout     vin     0      0      NMOS L=1 W=10 M2       vout     vin     vdd     vdd    PMOS L=1
W=200
* 50nm BSIM4 models
```


 
```
*Stage3 Inverter
.control destroy all run
let Icross=-i(vdd)
*plot Icross plot vout Vin
.endc
.option scale=50n
.dc vin 0 1 1m
vdd      vdd      0      DC      1
Vin      vin      0      DC      0
M1       vout     vin     0      0      NMOS L=1 W=10 M2      vout     vin     vdd     vdd     PMOS L=1
W=400
* 50nm BSIM4 models
```



```

*Three inverters in series
.control destroy all run
plot vout vin
.endc
.option scale=50n
.dc vin 0 1 1m

```

```


vdd    vdd      0      DC    1
Vin    vin      0      DC    0
M1     vout1    vin     0     0     NMOS L=1 W=10
M2     vout1    vin     vdd    vdd    PMOS L=1 W=20
M3     vout2    vout1    0     0     NMOS L=1 W=10
M4     vout2    vout1    vdd    vdd    PMOS L=1 W=200
M5     vout     vout2    0     0     NMOS L=1 W=10
M6     vout     vout2    vdd    vdd    PMOS L=1 W=400

```

```

* 50nm BSIM4 models
* Don't forget the .options scale=50nm if using an Lmin of 1
* 1<Ldrawn<200 10<Wdrawn<10000 Vdd=1V
* Change to level=54 when using HSPICE

```

 

Notice the switching point of the 3stage inverters is around 500mv though the second and third stage switching points are at 640mv.

12.2 (Logic Gate Design and Simulation)

Solution: A half adder circuit calculates a half sum (HS) and a carry out (CO). It takes two input bits, A and B. The logic equations for HS and CO are

$$HS = A \oplus B$$

$$CO = A \cdot B = \overline{(\overline{A} + \overline{B})}$$

Figure 1 shows a circuit schematic of a half adder's components. For clarity, the components are not wired together in the figure. The SPICE simulation and code appear on the next page.


 


Figure 1: Half adder components

 

*** Problem 12.2 ***

```
.control
destroy all
run
plot VA VB CO HS
.endc
```

```
.option scale=50n
.tran 10p 2.2n
```

```
Vdd      Vdd      0      DC      1
VA        VA        0      DC      0      pulse 0 1 250p 50p 50p 0.5n 1n
VB        VB        0      DC      0      pulse 0 1 1.5n 50p 50p 0.5n 1n
```

*XOR gate -- A XOR B = HS

```
M12      N3      VB      Vdd      Vdd      PMOS L=1 W=20
M11      HS      B_      N3      Vdd      PMOS L=1 W=20
```

```
M10      N3      VA      Vdd      Vdd      PMOS L=1 W=20
M9       HS      A_      N3      Vdd      PMOS L=1 W=20
```

```
M8       HS      A_      N2      0        NMOS L=1 W=10
M7       N2      B_      0        0        NMOS L=1 W=10
```

```
M6       HS      VA      N1      0        NMOS L=1 W=10
M5       N1      VB      0        0        NMOS L=1 W=10
```

*A inverter

```
M2       A_      VA      Vdd      Vdd      PMOS L=1 W=20
M1       A_      VA      0        0        NMOS L=1 W=10
```

*B inverter

```
M4       B_      VB      Vdd      Vdd      PMOS L=1 W=20
M3       B_      VB      0        0        NMOS L=1 W=10
```

*NOR gate -- A_ NOR B_ = AB = CO

```
M16      N4      A_      Vdd      Vdd      PMOS L=1 W=20
M15      CO      B_      N4      Vdd      PMOS L=1 W=20
M14      CO      B_      0        0        NMOS L=1 W=10
M13      CO      A_      0        0        NMOS L=1 W=10
```

```
.MODEL NMOS NMOS LEVEL = 14
.MODEL PMOS PMOS LEVEL = 14
```

```
.end
```